
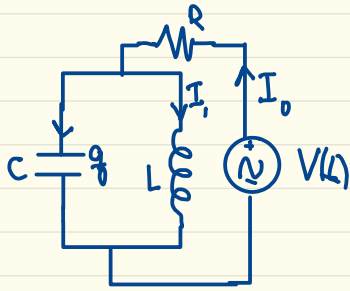


Lecture 19

Resonance in
Electrical
Circuits



Example: LC-Circuit



$$\begin{cases} R I_0 + \frac{q}{C} = V(t) \\ R I_0 + L \frac{dI_0}{dt} = V(t) \\ I_1 = I_0 - \frac{dq}{dt} \end{cases}$$

$$\begin{cases} I_0 = \frac{1}{R} \{V(t) - q/C\} \\ R I_0 + L \frac{dI_0}{dt} = V(t) \\ I_1 = I_0 - \frac{dq}{dt} \end{cases} \Rightarrow \begin{cases} R I_0 + L \frac{d}{dt} (I_0 - \frac{dq}{dt}) = V(t) \\ I_0 = \frac{1}{R} \{V(t) - q/C\} \end{cases}$$

$$R \frac{1}{R} \{V(t) - q/C\} + L \frac{d}{dt} \left(\frac{1}{R} \{V(t) - q/C\} - \frac{dq}{dt} \right) = V(t)$$

$$\cancel{R \frac{1}{R}} \{V(t) - q/C\} + L \frac{d}{dt} \left(\frac{1}{R} \{V(t) - q/C\} - \frac{dq}{dt} \right) = \cancel{V(t)}$$


$$-q/C + \frac{L}{R} \frac{dV(t)}{dt} - \frac{L}{RC} \frac{dq}{dt} - \frac{L}{R} \frac{d^2q}{dt^2} = 0$$

$$L \frac{d^2q}{dt^2} + \frac{L}{RC} \frac{dq}{dt} + q/C = \frac{L}{R} \frac{dV(t)}{dt} \quad q = CV$$

$$LC \frac{d^2V}{dt^2} + \frac{L}{R} \frac{dV}{dt} + V = \frac{L}{R} \frac{dV(t)}{dt}$$

$$\frac{d^2V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{1}{LC} V = \frac{1}{RC} \frac{dV(t)}{dt}$$

Example: LC-circuit (continued)

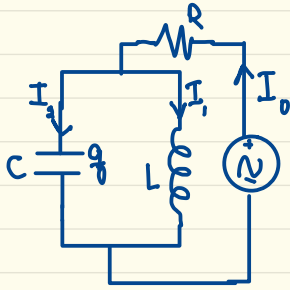

$$\frac{d^2 V_C}{dt^2} + \frac{1}{RC} \frac{dV_C}{dt} + \frac{1}{LC} V_C = \frac{1}{RC} \frac{dV(t)}{dt}$$

$$V(t) = \cos(\omega t)$$

Frequency response:

$$\left\{ -\omega^2 + \frac{1}{RC} i\omega + \omega_0^2 \right\} G e^{i\omega t} = \frac{i\omega e^{i\omega t}}{RC}$$

$$\begin{aligned} \text{So } G(i\omega) &= \frac{i\omega/RC}{(\omega_0^2 - \omega^2) + i\omega/RC} \\ &= \frac{1}{\frac{\omega_0^2 - \omega^2}{i\omega/RC} + 1} = \frac{1}{1 + RC \frac{(\omega_0^2 - \omega^2)}{\omega} i} \end{aligned}$$





Resonance at $\omega = \omega_0 = \frac{1}{\sqrt{LC}}$, $\varphi = 0$

$$\omega_0 = \frac{1}{\sqrt{LC}} \approx 6.45 \times 10^4$$

$$f_0 = \frac{\omega_0}{2\pi} \approx 10.27 \times 10^3$$

$$\approx 10.3 \text{ kHz}$$
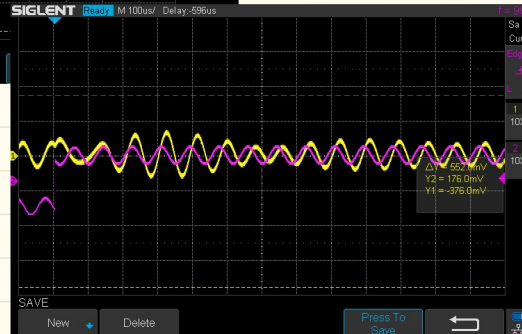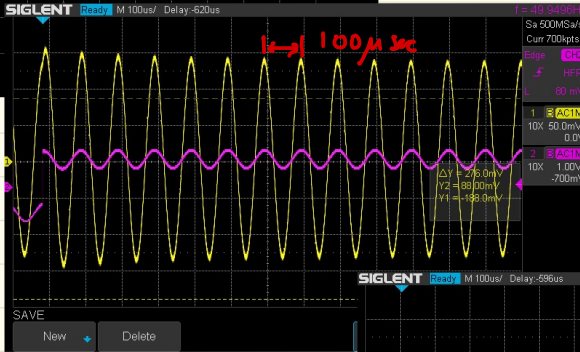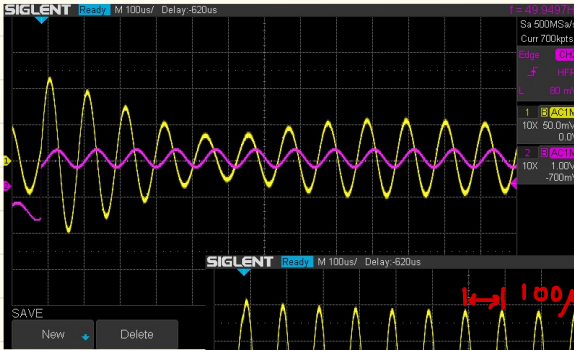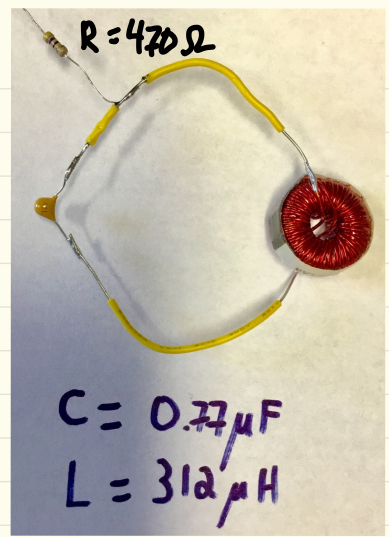
$$\text{Period} = \frac{1}{f_0} \approx 97 \times 10^{-6} \text{ sec.}$$



A.M. Radio

$$V_C'' + \frac{1}{RC} V_C' + \frac{1}{LC} V_C = \frac{1}{RC} V'(t)$$


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Frequency response:

$$\left\{ \omega^2 + \frac{1}{RC} i\omega + \omega_0^2 \right\} G e^{i\omega t} = \frac{i\omega e^{i\omega t}}{RC}$$


$$\text{So } G(i\omega) = \frac{\omega/RC}{(\omega^2 - \omega_0^2) + i\omega/RC} = \frac{1}{\frac{\omega^2 - \omega_0^2}{i\omega/RC} + 1} = \frac{1}{1 + RC \frac{(\omega^2 - \omega_0^2)}{\omega} i}$$

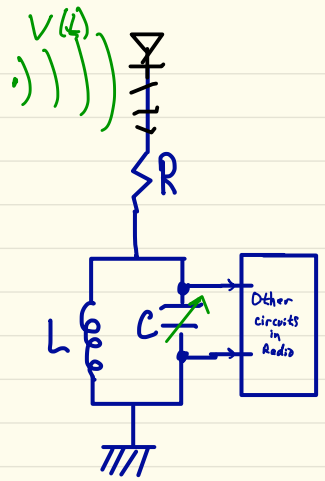Resonance at $\omega = \omega_0 = \frac{1}{\sqrt{LC}}$
 $\varphi = 0$



$$V_C(t) = R(\omega) \cos(\omega t - \varphi)$$

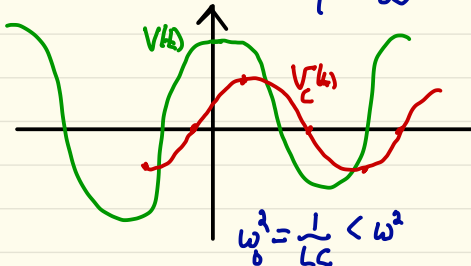
$$\varphi = \tan^{-1} \left\{ \frac{(\omega^2 - \omega_0^2) RC}{\omega} \right\}$$



$$V_c(t) = R(\omega) \cos(\omega t - \varphi)$$

$$R(\omega) = \frac{1}{\sqrt{1 + \left(\frac{\omega^2 - \omega_0^2}{\omega_0} RC\right)^2}}$$
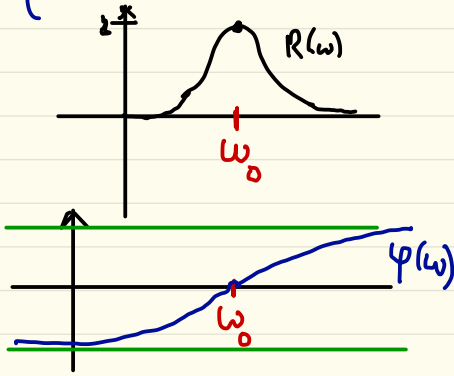
$$\varphi = \tan^{-1} \left\{ \frac{(\omega^2 - \omega_0^2) RC}{\omega} \right\}$$



$$L = 220 \mu\text{H}$$

$$27 \text{ pF} \leq C \leq 383 \text{ pF} \quad (383 \times 10^{-12} \text{ F})$$



$$R = 1000 \text{ Ohm}$$

$$f = \frac{\omega}{2\pi} = 700 \text{ kHz}$$

Note $\frac{1}{LC} = \omega_0^2$ so at resonance

$$C = \frac{1}{L \cdot \omega_0^2} \approx 2.35 \times 10^{-10} \text{ F}$$

$$\approx 235 \text{ pF}$$

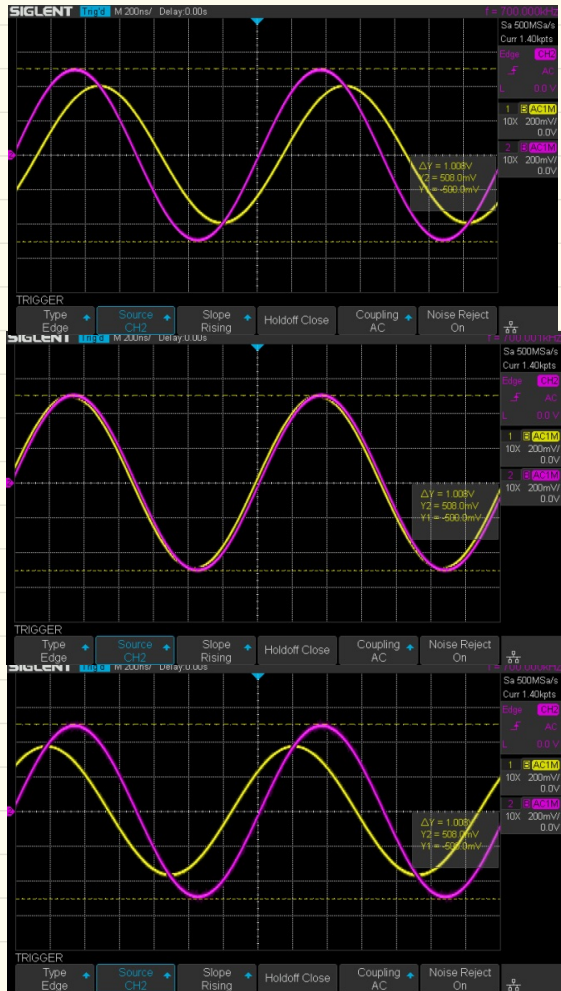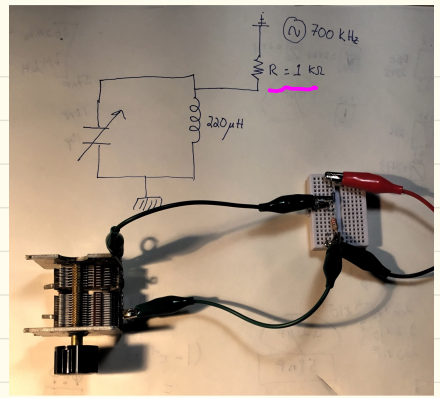

$$R(\omega) = \frac{1}{\sqrt{1 + \left(\frac{\omega^2 - \omega_0^2}{\omega_0 RC}\right)^2}} \quad \text{Gain}$$

